

Circuit Analysis I ELE1121

Course Given by

Emmanuel Wokulira Miyingo

Dept of ELE & Computer Engineering

Email: miyingo@yahoo.com


Mob: 0702423774/0782423774

Transient Signals

- Consider the circuit (next slide):
- A switch, which closes at a time $t = 0$ is included in a series circuit of R & C.
- In practice, this is done; otherwise the practical analysis (using an oscilloscope) is not possible.

Transient Signals: R-C Circuit

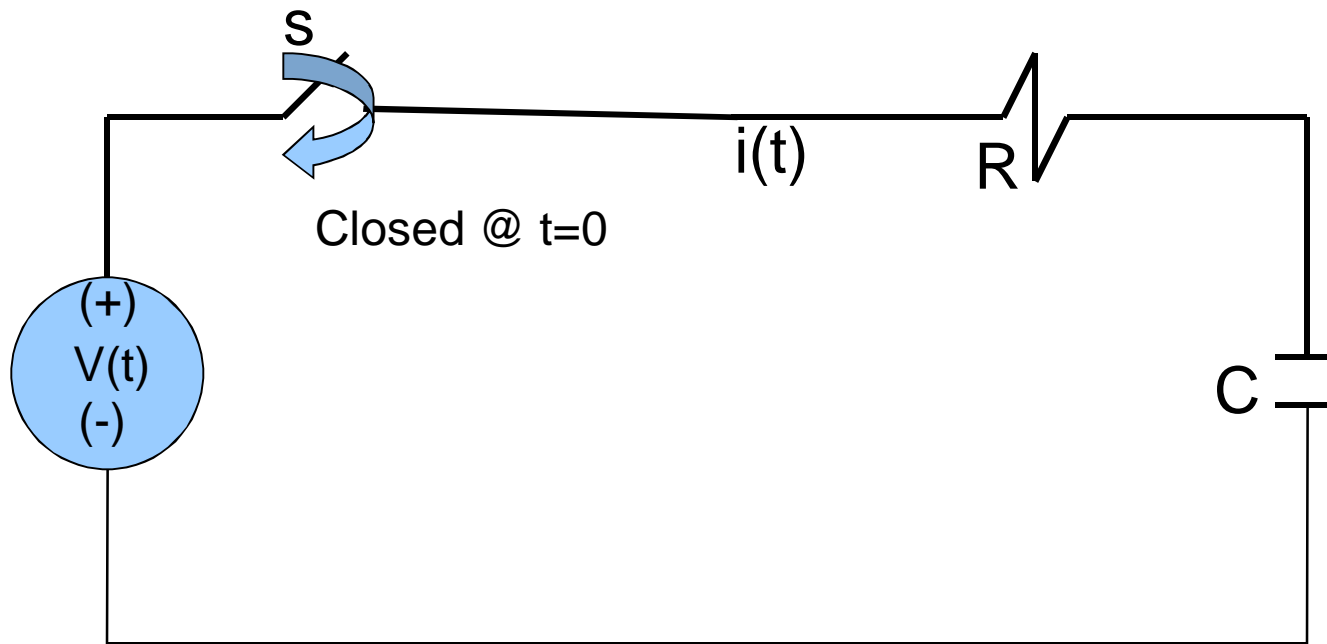- A capacitive circuit is modified to include a switch:



Transient Signals: R-C Circuit

- From the knowledge of capacitor behaviour; it will act as a short @ $t = 0$, & open circuit as $t \rightarrow \infty$

clearly;

$$i_0 = \frac{V_0}{R} = \text{current when } t = 0$$

$$i_\infty = 0 = \text{current when } t \rightarrow \infty$$

Transient Signals: R-C Circuit Cont'd

- It is in our interest to find

values of i

$$0 \leq t \leq \infty;$$

*this is called transient current / response
of the circuit .*

When the switch (s) is closed ;

$$i(t) = \frac{v(t)}{R + Z_C}$$

Transient Signals: R-C Circuit Cont'd

- We have 2 ways of determining $i(t)$:
 1. Using Laplace Transforms.
 2. Using Ordinary Differential Equations. DE Table
- In the interest of time we shall use Laplace


Let

$s = j\omega = \text{Laplace operator}$

$$\therefore Z = R + \frac{1}{j\omega C} = R + \frac{1}{sC}$$

Transient Signals: R-C Circuit Cont'd

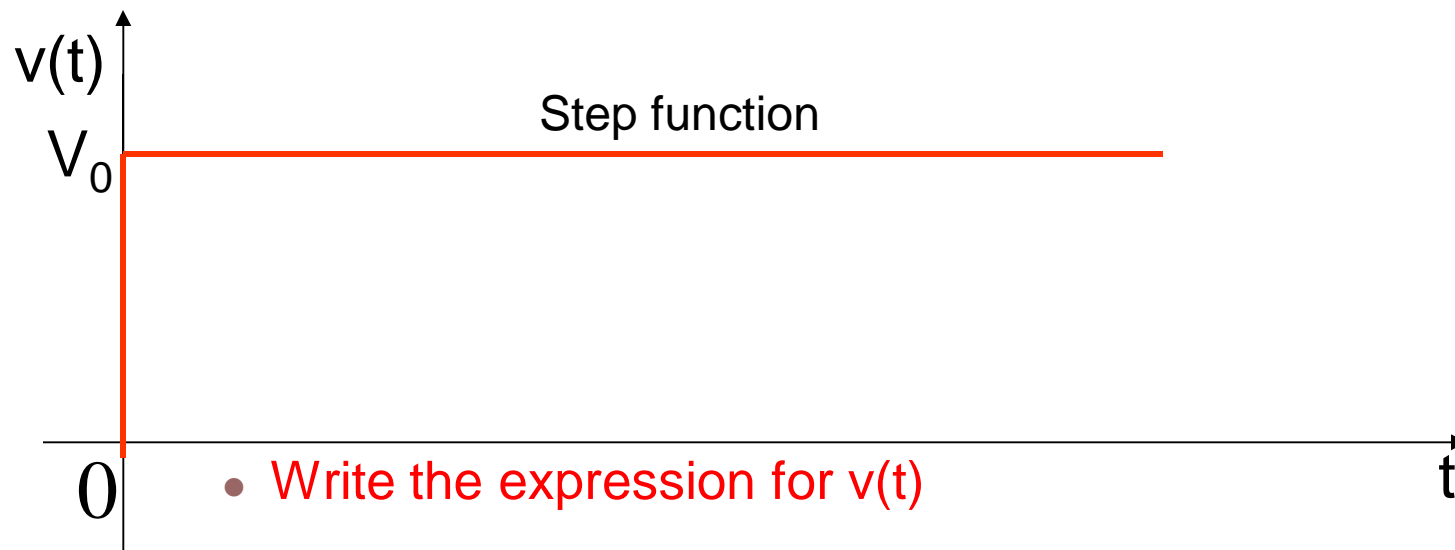- The operation of suddenly closing the switch results in a voltage waveform below



Transient Signals: R-C Circuit Cont'd

- Thus $v(t)$ is a Step Function of magnitude V_p
- The Laplace transform of the step function voltage above and the Laplace transform of the current are given by: Recall: Transformation Table

$$V(s) = \frac{V_0}{s}$$

$$\therefore I(s) = \frac{\frac{V_0}{s}}{R + \frac{1}{sC}} = \frac{V_0 C}{sCR + 1}$$

Transient Signals: R-C Circuit Cont'd

$$\therefore I(s) = \frac{V_0}{R} \cdot \frac{1}{s + \frac{1}{CR}}$$

Transform Table

*\therefore Inverse Laplace Transform of $I(s)$
is $i(t)$ given by :*

$$i(t) = \frac{V_0}{R} \cdot [e^{-\frac{t}{CR}}]u(t)$$

Inverse Laplace Transform (Standard Signal)

- Recall: the Laplace Transform \leftrightarrow Inverse Laplace Transform Table:

$$\text{if } I(s) = \frac{1}{s + a}$$

i(t) is given by :

$$i(t) = e^{-at} u(t)$$

Inverse Laplace Transform (Standard Signal) Cont'd

- the Inverse Laplace Transform of:

$$\text{similarly } I(s) = \frac{1}{s+a} + \frac{1}{s+b}$$


i(t) is given by :

$$i(t) = [e^{-at} + e^{-bt}]u(t)$$

Transient Signals: R-C Circuit

- We can easily check for the initial & final values of $i(t)$ by substituting for values of t .
- We can also sketch i vs. t .
- The results confirm our previous knowledge of a charging capacitor.

Transient Signals: R-C Circuit Cont'd

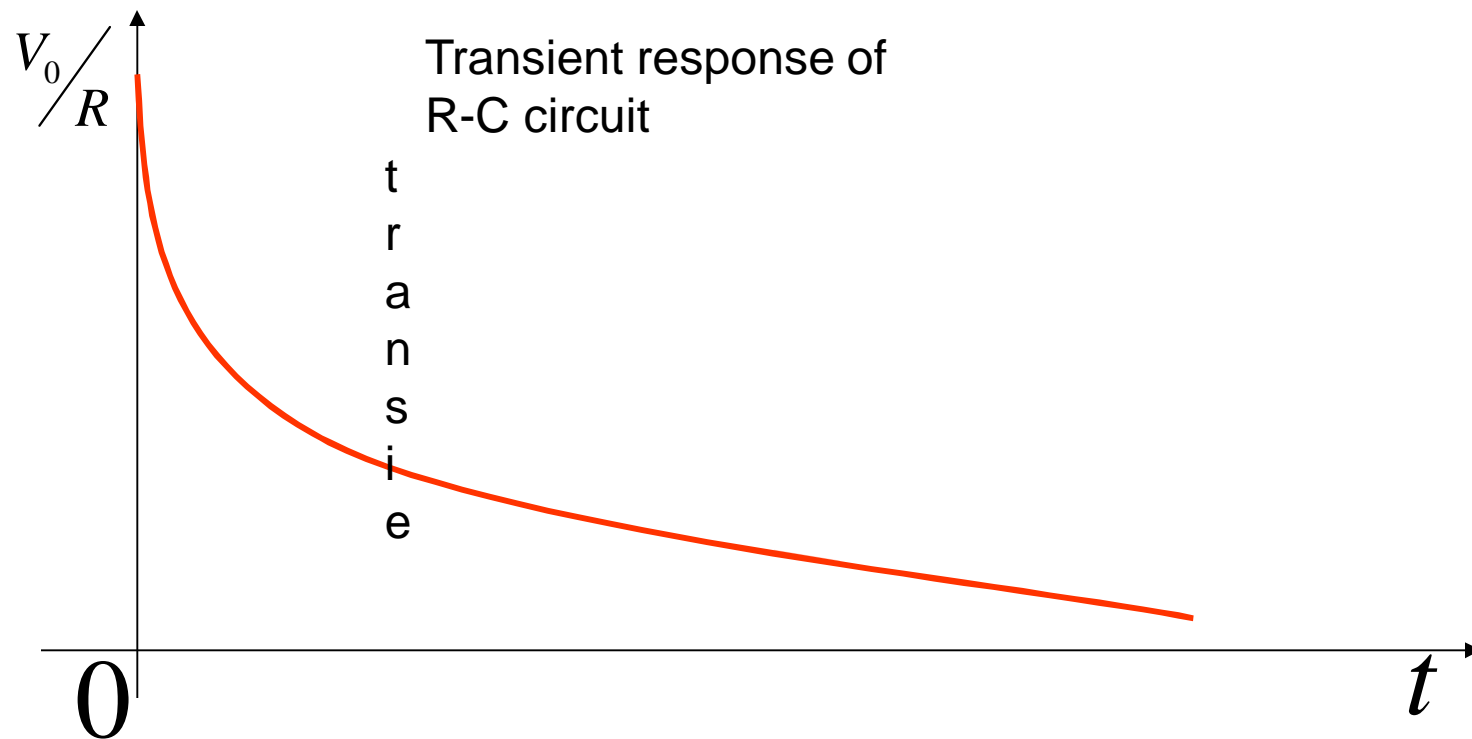


Transient Signals: R-L Circuit

- Similarly, let us consider the transient behaviour of an R-L circuit next slide:
- The same conditions apply:
 1. Switch s is closed suddenly.
 2. The signal received by R & L is a step function shown above.

Transient Signals: R-L Circuit Cont'd

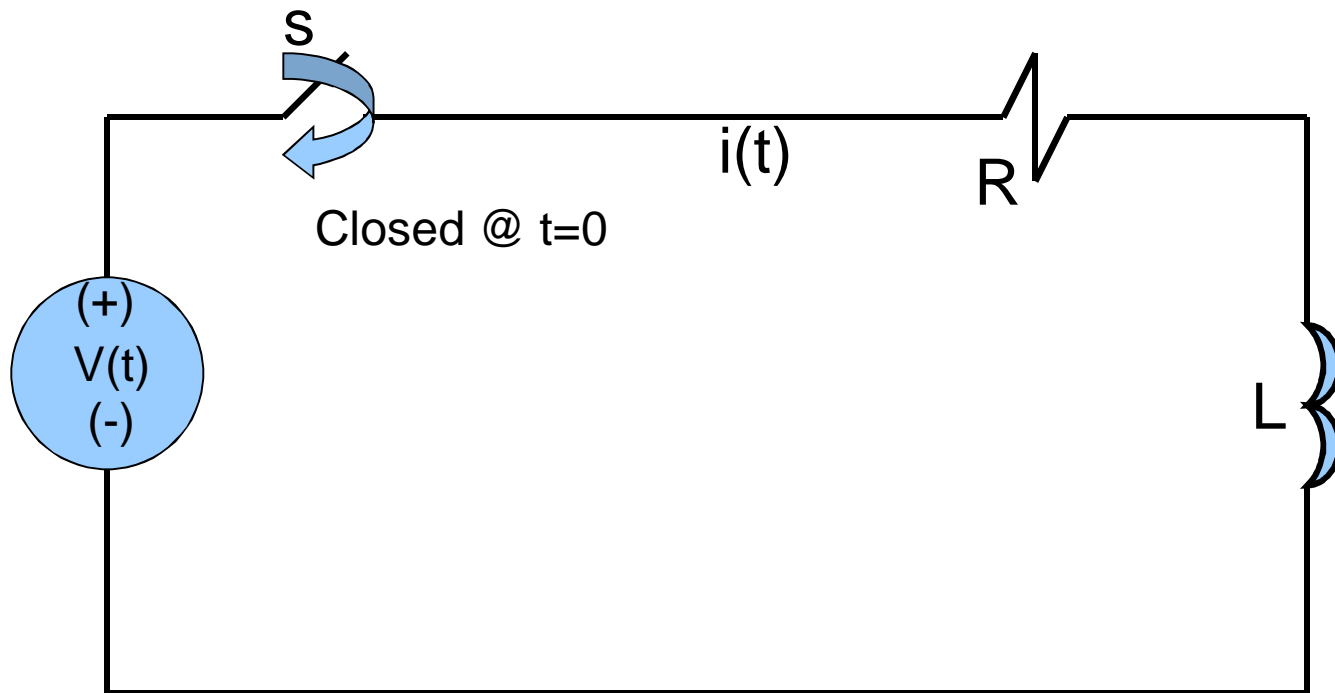- An inductive circuit is modified to include a switch:



Transient Signals: R-L Circuit

Cont'd

- From the knowledge of inductor behaviour; it will act as open @ $t = 0$, & short circuit as

$$t \rightarrow \infty$$

clearly;

$$i_0 = 0 = \text{current when } t = 0$$

$$i_\infty = \frac{V_0}{R} = \text{current when } t \rightarrow \infty$$

Transient Signals: R-L Circuit Cont'd

- The Laplace Transforms are as follows:
- The Laplace transform of the step function voltage above and the Laplace transform of the current are given by:

$$V(s) = \frac{V_0}{s}$$

$$Z = R + j\omega L;$$

$$Z(s) = R + sL$$

$$\therefore I(s) = \frac{V_0/s}{R + sL} = \frac{V_0}{s[R + sL]}$$

Transient Signals: R-L Circuit

Cont'd

- Using Partial Fractions

- $$I(s) = \frac{V_0}{s(R+sL)} \equiv V_0 \left[\frac{A}{s} + \frac{B}{(R+sL)} \right]$$

- Determining A and B

- $$A = \frac{1}{R} \text{ and } B = -\frac{L}{R}$$

- $$\therefore I(s) = \frac{V_0}{R} \left[\frac{1}{s} - \frac{L}{(R+sL)} \right] = \frac{V_0}{R} \left[\frac{1}{s} - \frac{1}{(s+R/L)} \right]$$


Transient Signals: R-L Circuit Cont'd

- The transient current is obtained from the Inverse Laplace Transform of $I(s)$ to give $i(t)$.

$$i(t) = \frac{V_0}{R} (1 - e^{-(R/L)t}) u(t)$$


- We can again check the initial & final values of $i(t)$ & also plot $i(t)$ v's t .

Transient Signals: R-L Circuit Cont'd

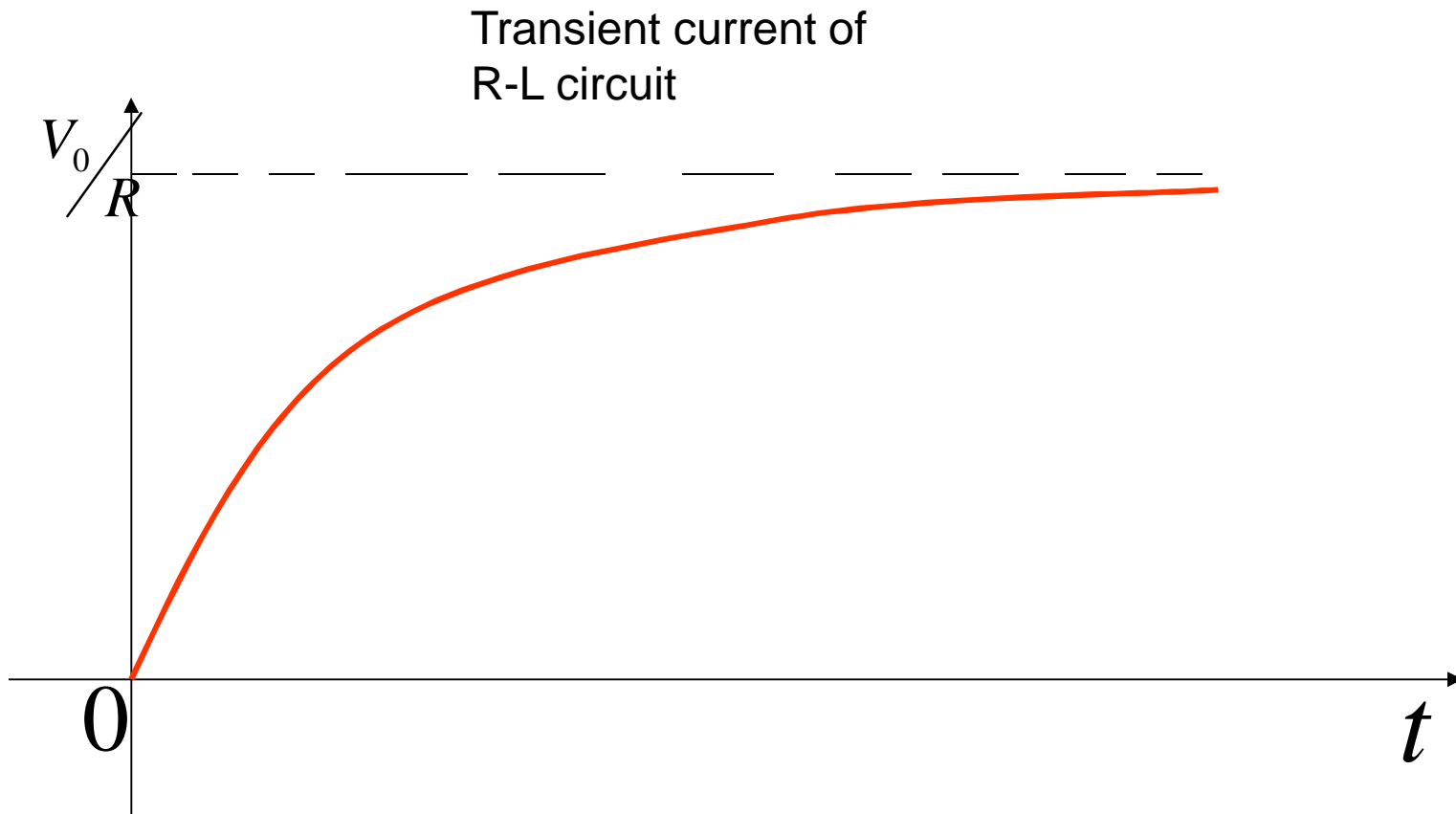

Transient Signals: R-L-C Circuit

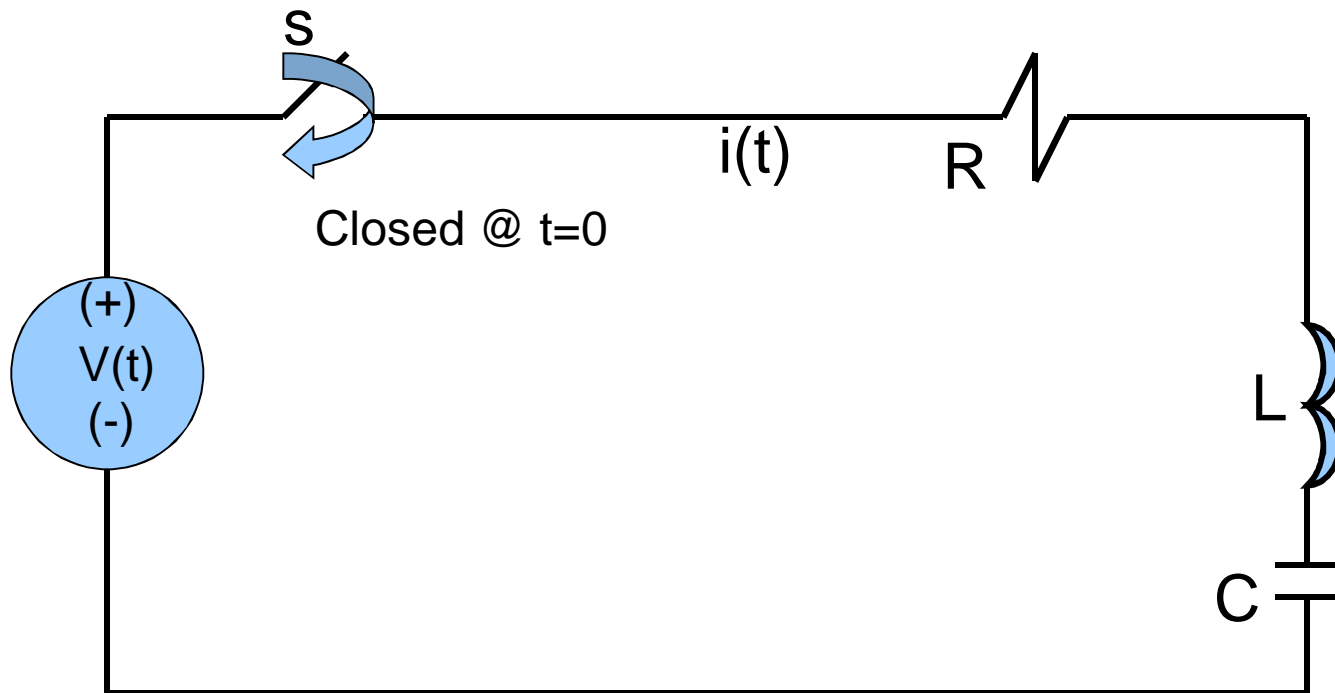- A circuit is designed to include R, L, & C



Transient Signals: R-L-C Circuit Cont'd

$$Z(s) = R + sL + \frac{1}{sC}$$

$$Z(j\omega) = R + j\omega L - j\frac{1}{\omega C}$$

\therefore There is a critical freq $= \omega_{cr}$

$$= \omega_{cr} = \frac{1}{\sqrt{LC}}$$

$$\therefore Z(\omega_{cr}) = R$$

Transient Signals: R-L-C Circuit Cont'd

We can show that :

$$\frac{V_0}{s} = I(s) \left[R + sL + \frac{1}{Cs} \right]$$

$$\therefore I(s) = \frac{V_0 C}{LCs^2 + RCs + 1}$$

$$\equiv \frac{V_0 C}{bs^2 + as + 1}; \text{ where } a = RC, b = LC$$

Transient Signals: R-L-C Circuit Cont'd

- We can solve the quad equation below for two values of s :

$$bs^2 + as + 1 = 0$$

$$s = \frac{-a \pm \sqrt{a^2 - 4b}}{2b}$$

\therefore if

$(a^2 - 4b) > 0$; *real roots of s*

$(a^2 - 4b) = 0$; *repeated roots of s*

$(a^2 - 4b) < 0$; *complex roots of s*

Transient Signals: R-L-C Circuit Cont'd

Alternatively, we may solve the quad eqn

$$s^2 LC + RCs + 1 = 0$$

$$\therefore s_1, s_2 = \frac{-RC \pm \sqrt{(R^2 C^2 - 4LC)}}{2LC}$$

\therefore Depending on values of R, L & C ;

s_1, s_2 may be real or complex

Transient Signals: R-L-C Circuit Cont'd

- We may obtain the Inverse Laplace Transform of $I(s)$ to obtain $i(t)$ for the two cases where roots of s are real or complex.
- Let us write the expression of $I(s)$ as:

$$\frac{V_0 C}{1 + as + bs^2} = \frac{V_0 C}{(s - s_1)(s - s_2)}$$

Transient Signals: R-L-C Circuit Cont'd

$$\therefore \frac{I(s)}{V_0 C} = \frac{1}{(s - s_1)(s - s_2)}$$

By partial fractions;

$$\frac{1}{(s - s_1)(s - s_2)} \equiv \frac{A}{s - s_1} + \frac{B}{s - s_2}$$

$$\therefore A = \frac{1}{s_1 - s_2}, B = \frac{1}{s_2 - s_1}; A = -B$$

Transient Signals: R-L-C Circuit Cont'd

∴ By Inverse Laplace Transform;

$$i(t) = V_0 CA(e^{s_1 t} - e^{s_2 t})u(t)$$

Clearly,


$$i(0) = 0$$

$i(\infty) = 0$; if s_1, s_2 have negative real parts;


we can show that it is true

Transient Signals: R-L-C Circuit Cont'd

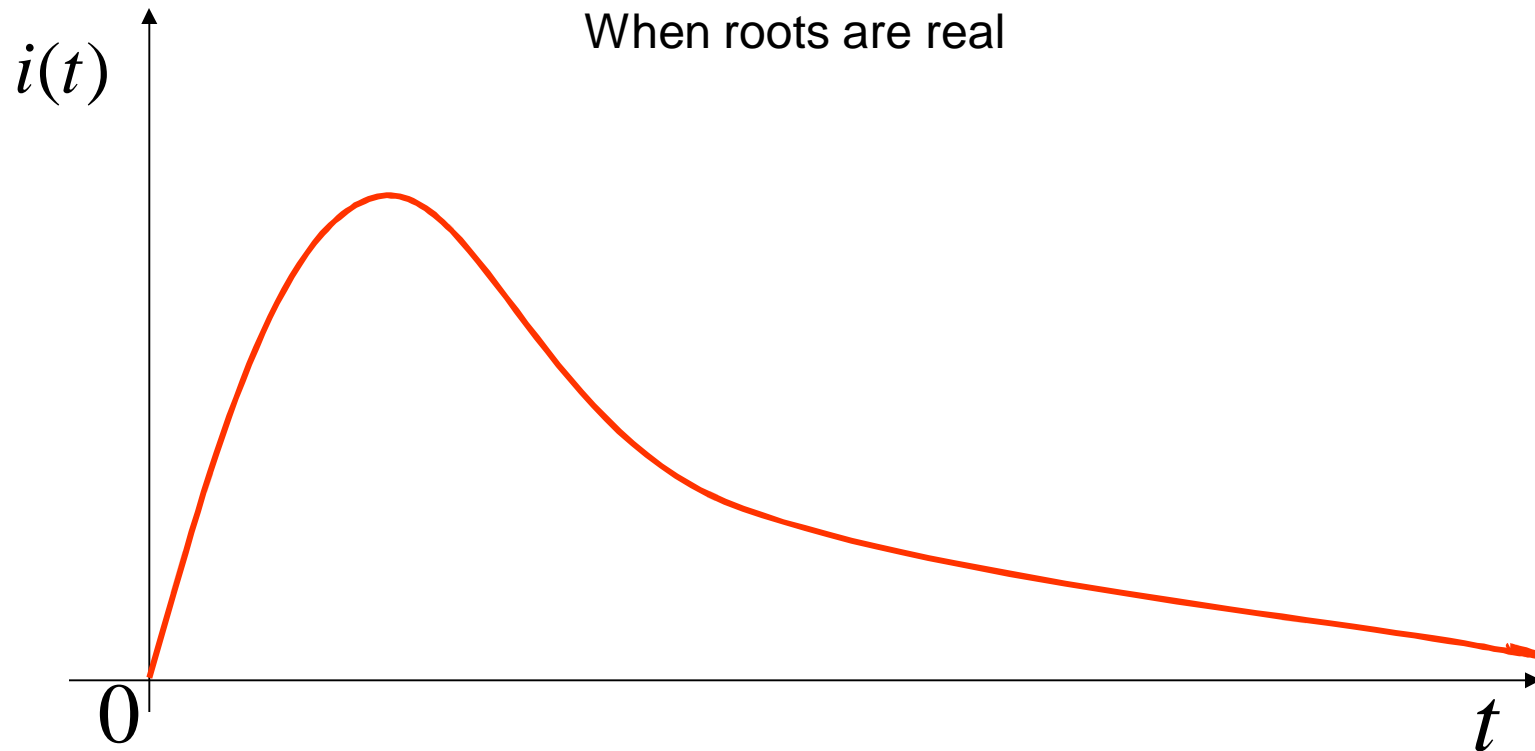- We can sketch $i(t)$ vs. t . Its general shape is:



Transient Signals: R-L-C Circuit Cont'd

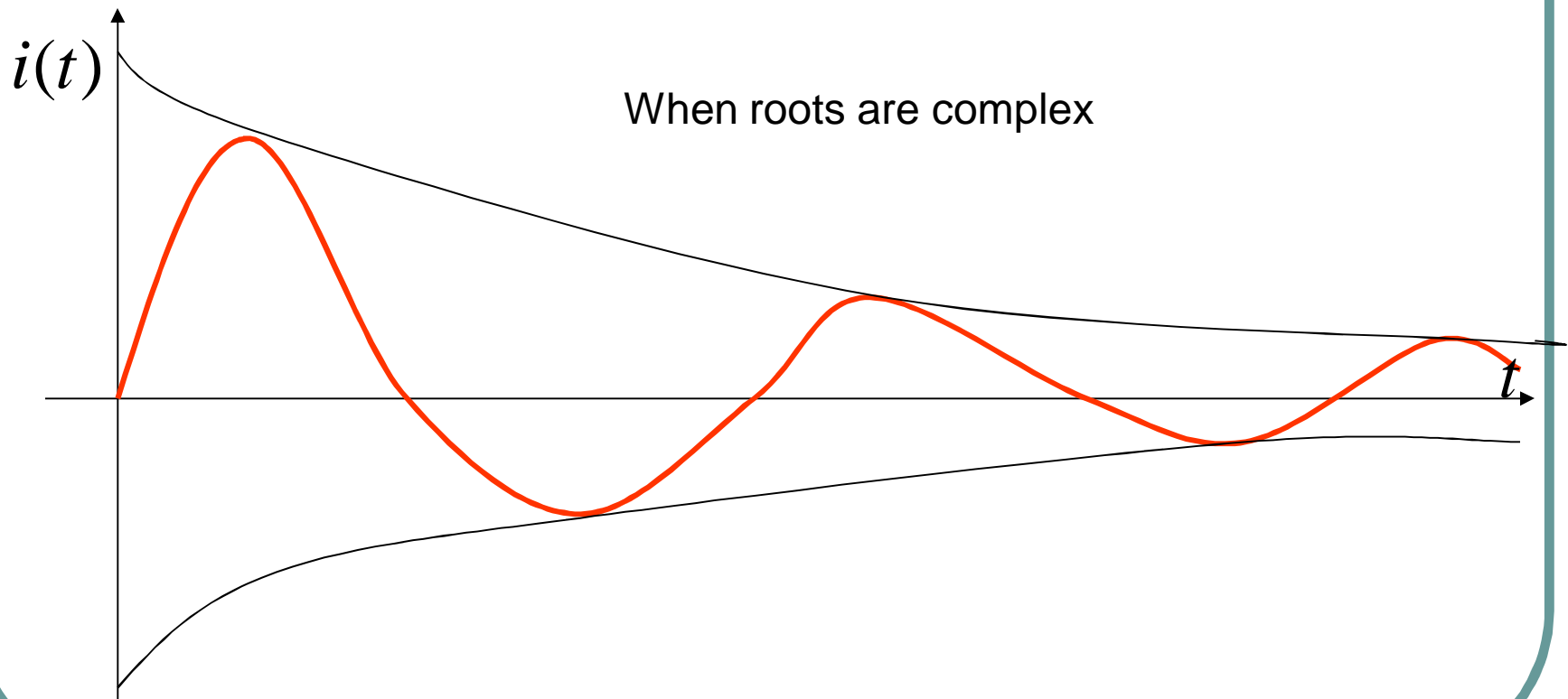


Transient Analysis of Circuits

- The above analysis of the transient response, analysed using the current $i(t)$, used the **step function** as the input signal.
- It is possible to consider, in general, the transient response of any given circuit due to different input signals.
- If response to a given input is analysed, we can fairly accurately determine the circuit elements & their connections.





Transient Analysis of Circuits Cont'd

Circuit

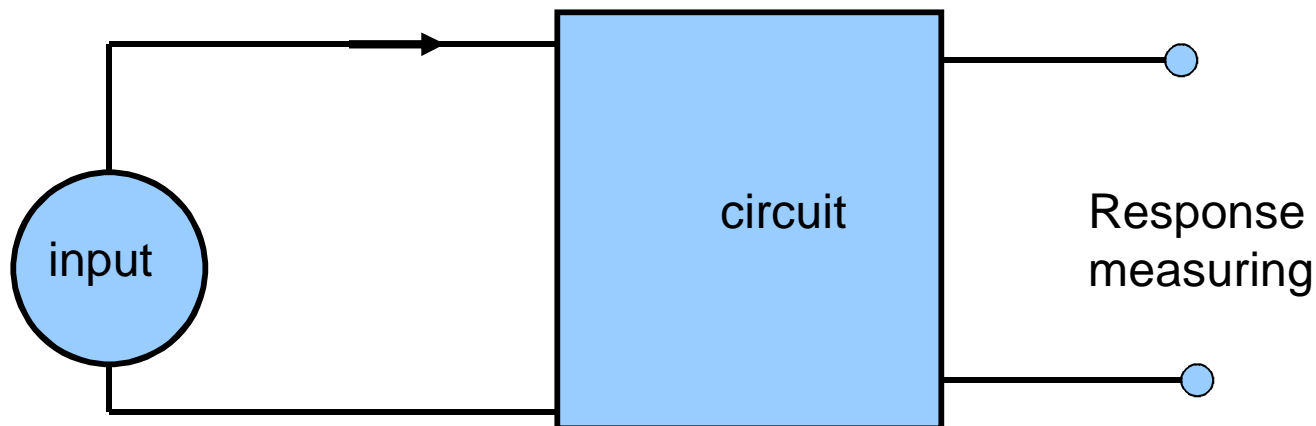

Standard Input Signals for Transient Analysis

- Input Signals

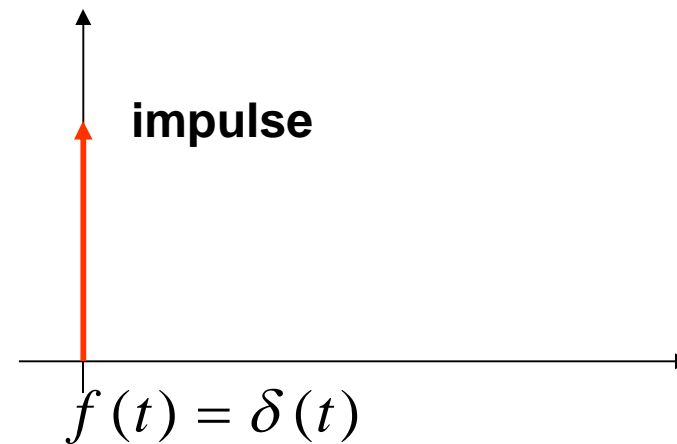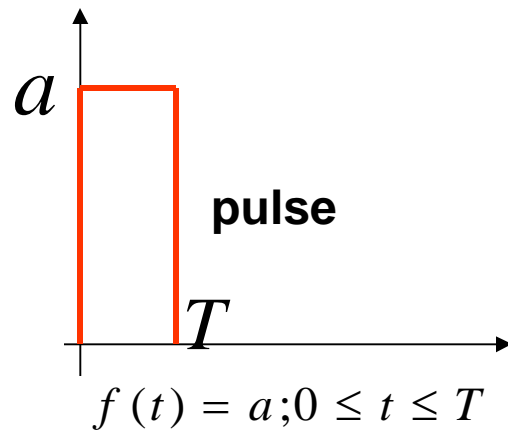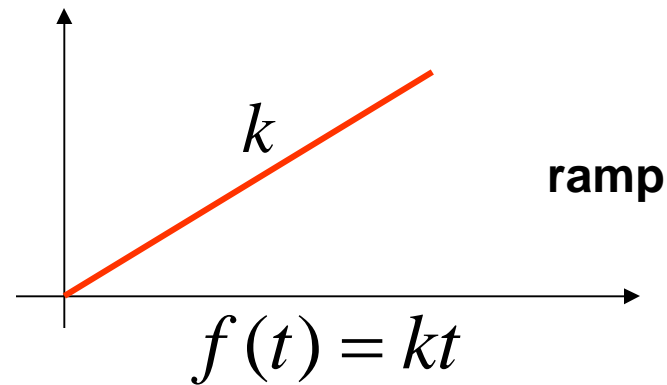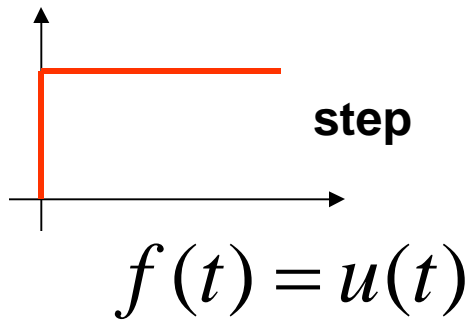


Input Signals

- It is possible to consider different inputs to the same circuit. Its response, as expected, will be different for each input.
- Consider the R-L circuit above and let the input signals be changed to
- (i) Impulse (ii) ramp (iii) pulse.

Transient Signals: R-L Circuit

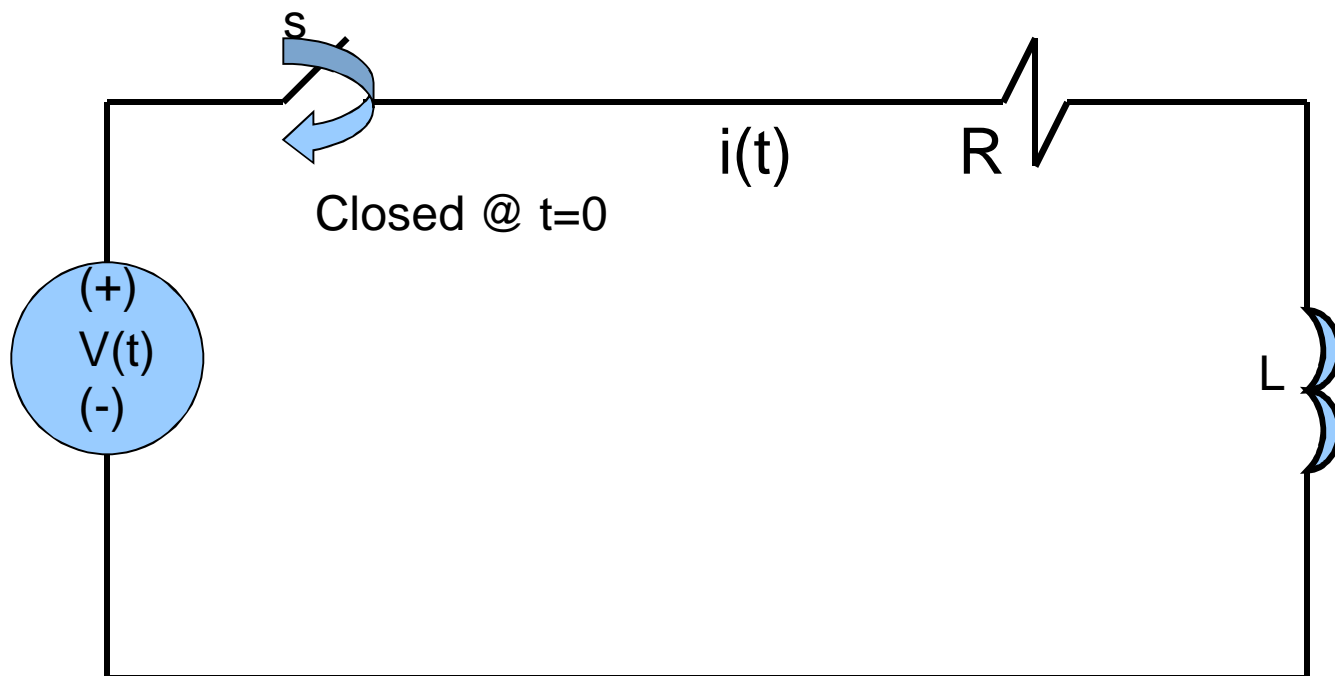- Let the voltage supply/input be an impulse.



Response of R-L Circuit to an Impulse Input

- By Laplace:

$$I(s) = \frac{V(s)}{R + sL}$$

But


$V(s) = \text{Laplace Transform of an impulse} = 1$

$$\therefore I(s) = \frac{1}{R + sL} = \frac{1/L}{s + R/L}$$

$$\therefore i(t) = \frac{1}{L} [e^{-Rt/L}] u(t)$$

Response of R-L Circuit to an Impulse Input Cont'd

- The transient response is:

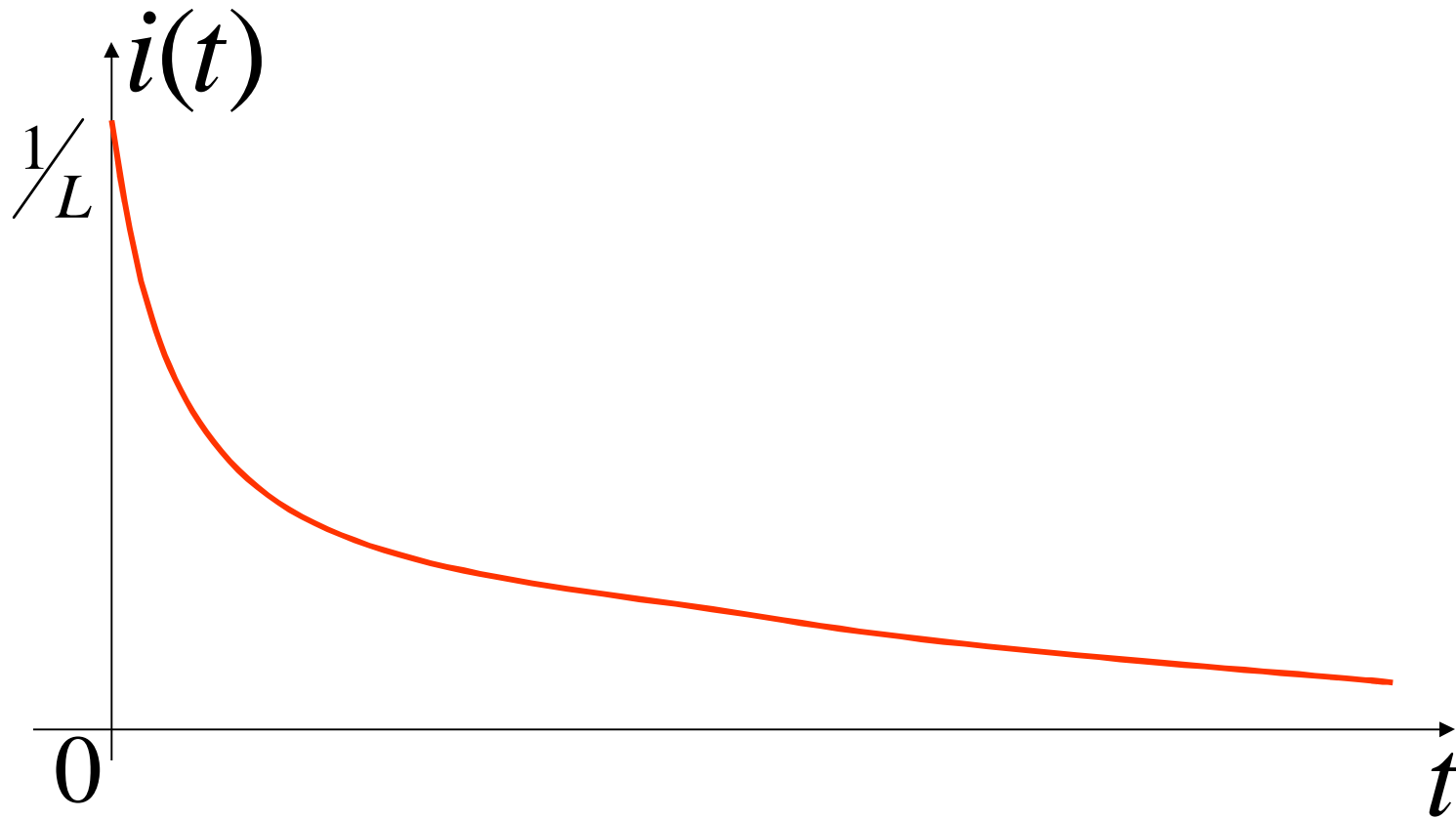

Response of R-L Circuit to a Ramp Input

- Consider the input to be a ramp of gradient k .
- Needless to redraw the circuit:

Laplace Transform of a ramp is :

$$\therefore I(s) = \frac{\frac{1}{s^2}}{R + sL} = \frac{1}{s^2(R + sL)}$$

Response of R-L Circuit to a Ramp Input Cont'd

$$\therefore \frac{1}{s^2(R + sL)} \equiv \frac{as + b}{s^2} + \frac{x}{R + sL}; \text{partial fract.}$$

$$1 \equiv (x + al)s^2 + (aR + bL) + bR$$

$$\therefore a = -L/R^2, b = 1/R, x = L^2/R^2$$

$$\therefore \frac{1}{s^2(R + sL)} = \frac{1}{R^2} \left[\frac{R}{s^2} - \frac{L}{s} + \frac{L}{s + R/L} \right]$$

Response of R-L Circuit to a Ramp Input Cont'd


$$\therefore i(t) = \frac{1}{R^2} [Rt - L + Le^{-Rt/L}] u(t)$$

We can deduce that :

$$i(0) = 0,$$


$$i(t)_{t \rightarrow \infty} = \frac{1}{R^2} [Rt] \equiv \text{ramp}$$

Response of R-L Circuit to a Ramp Input

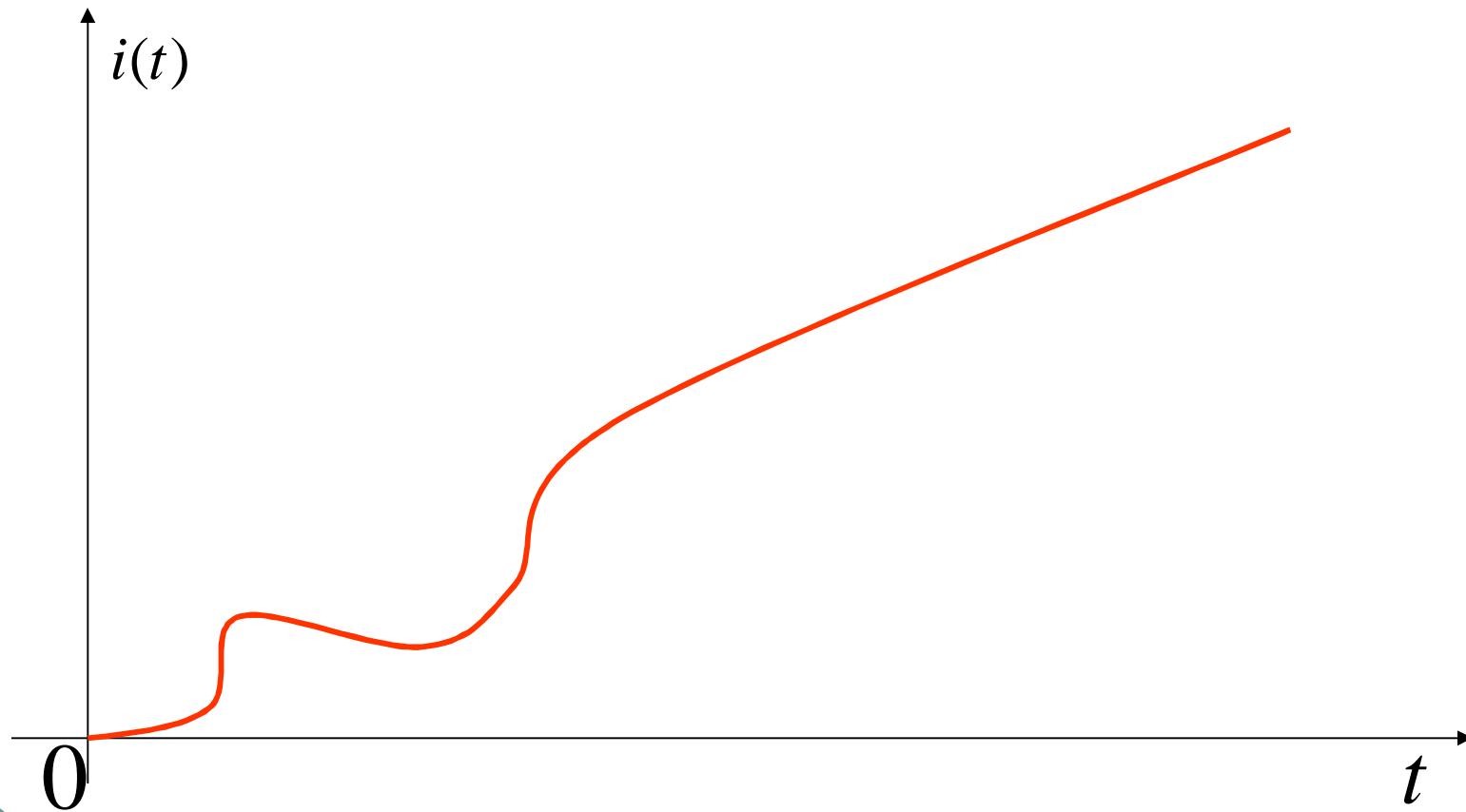

Response of R-L Circuit to a Pulse Input

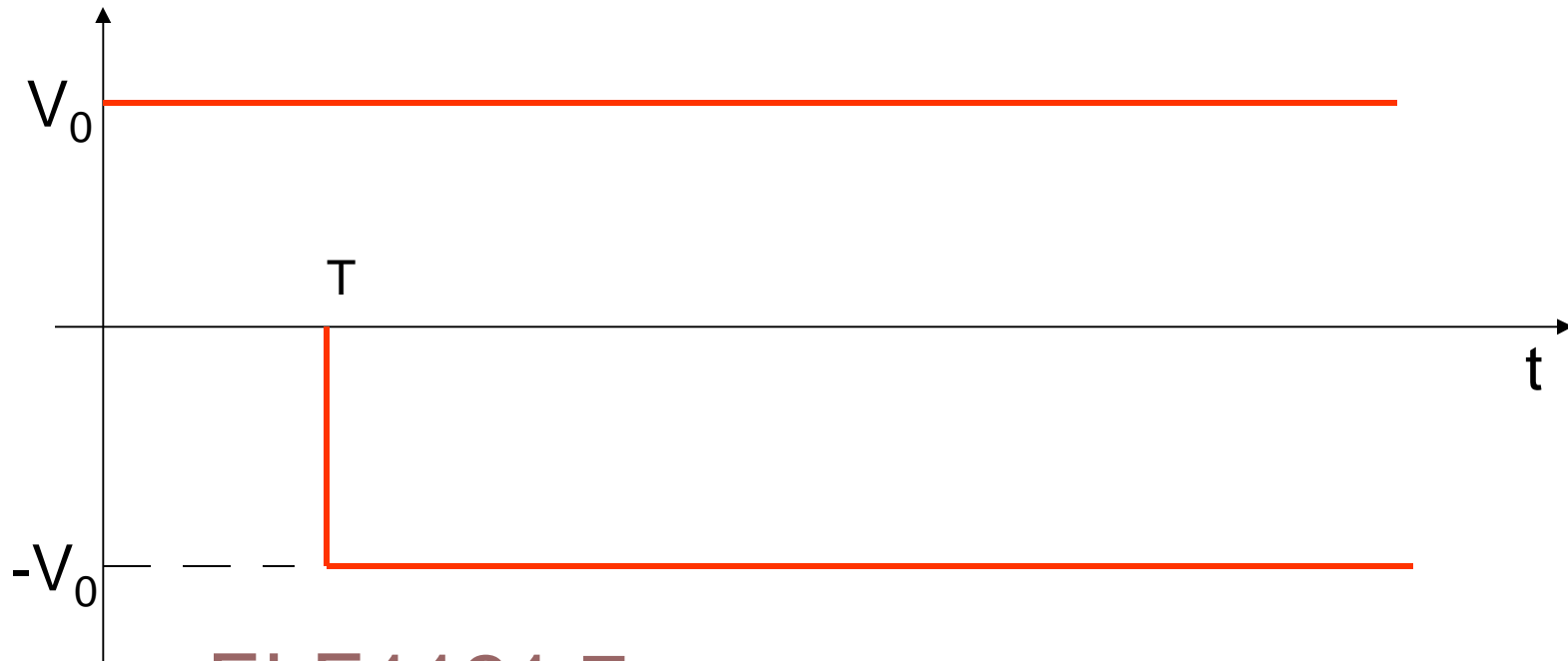- The pulse input may be considered as two steps; where one is delayed by time T .



ELE1121 7